

GAJENDRA-I



Professor -Ayon Chakraborty

Contributors-

1. Dev Mehta-CS22B007
2. Shreyas Bargale-CS22B016

Features of Gajendra-I CPU-

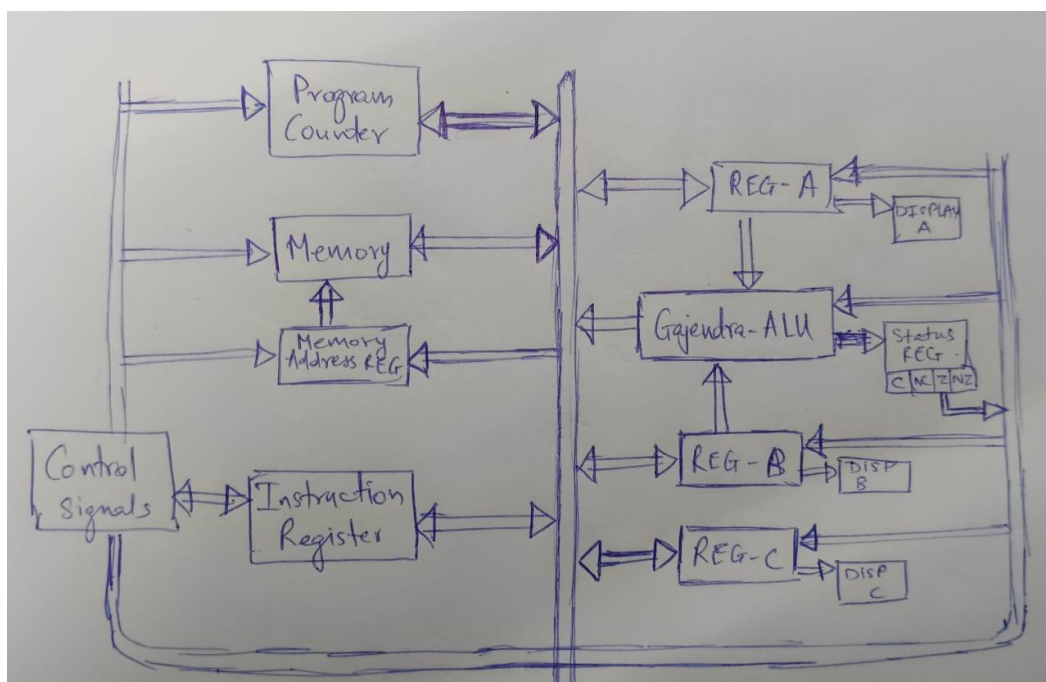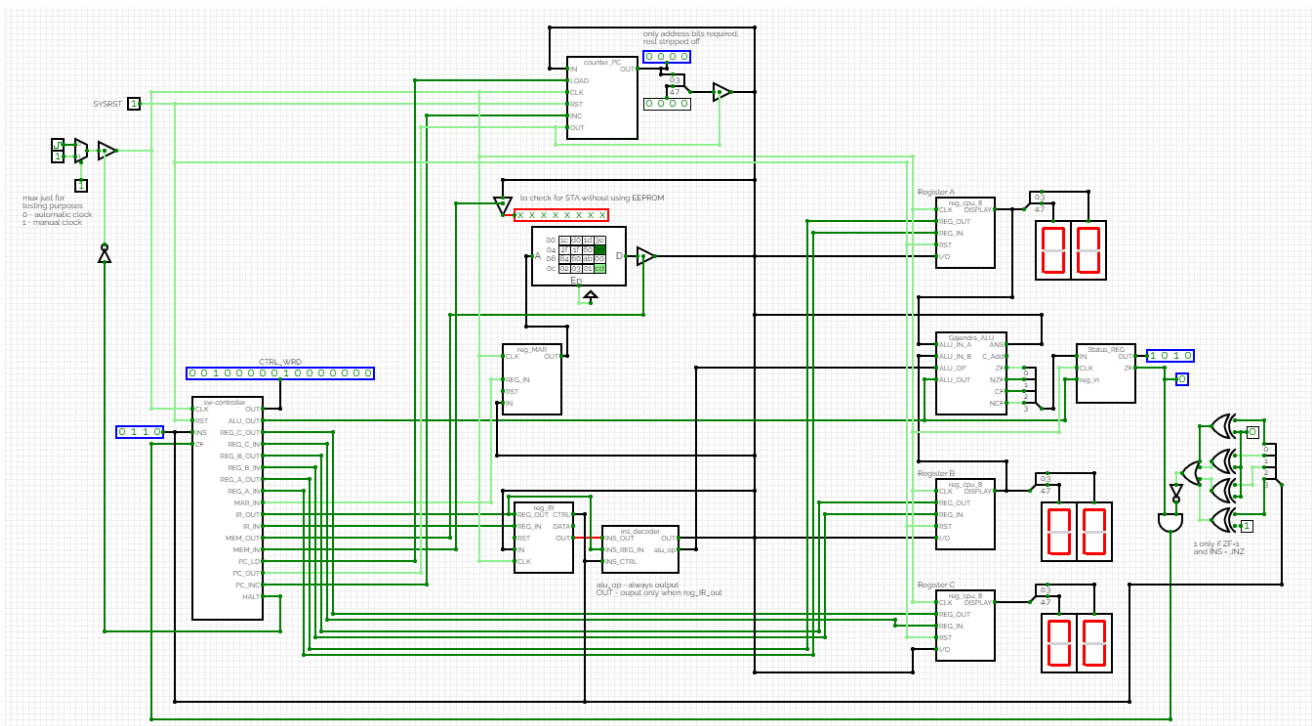
1. Supports 16 bytes of memory(ROM)
2. Recommended 8 locations of program space and 8 locations of data space.
3. CPU has an 8 bit bus which carries both instructions and data.
4. 8 bit ALU for arithmetic operations
5. Software controller used for controlling the execution of program.
6. Also implemented FSM controller (but with fewer instructions).
7. Instructions-
 - Supports instructions like CMP(compare), SWAP, MOV instructions, SHIFT (Left/Right).
 - Supports STA
 - Supports add, subtract, load, etc.
 - Supports JNZ.(Jump if not zero)



COMPONENTS OF GAJENDRA-I

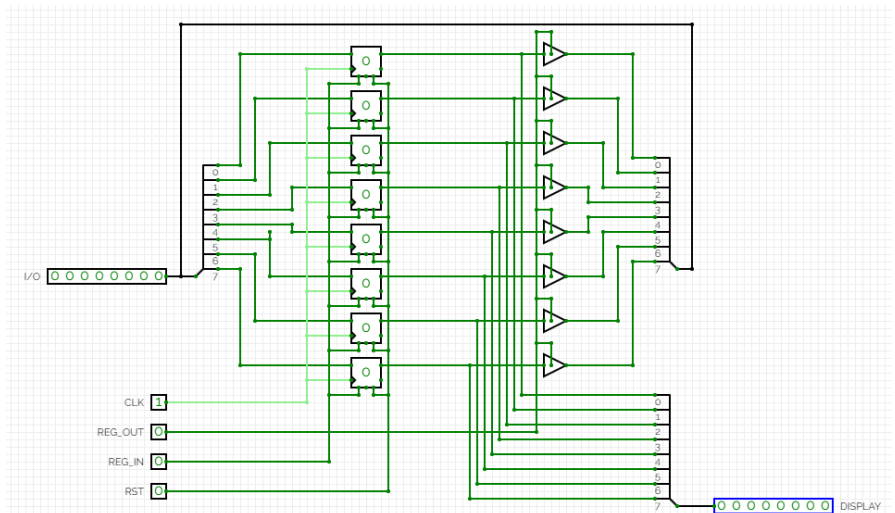1. General CPU registers (reg_cpu_8)

- General CPU registers are used to store data on which operations like ADD, SUB, CMP, left shift, right shift are to be performed.
- Data can also be transferred between the General CPU registers through operations like SWAP and MOV.



I/O : common input/output bus (8 bit)

REG_IN : if 1, register takes input from the bus

REG_OUT : if 1, register gives output to the bus


(Note : both REG_IN & REG_OUT must not be 1 together)

RST : resets all bits (D - flip flops) to 0

CLK : clock controlling the D - flip flops (connected to system clock)

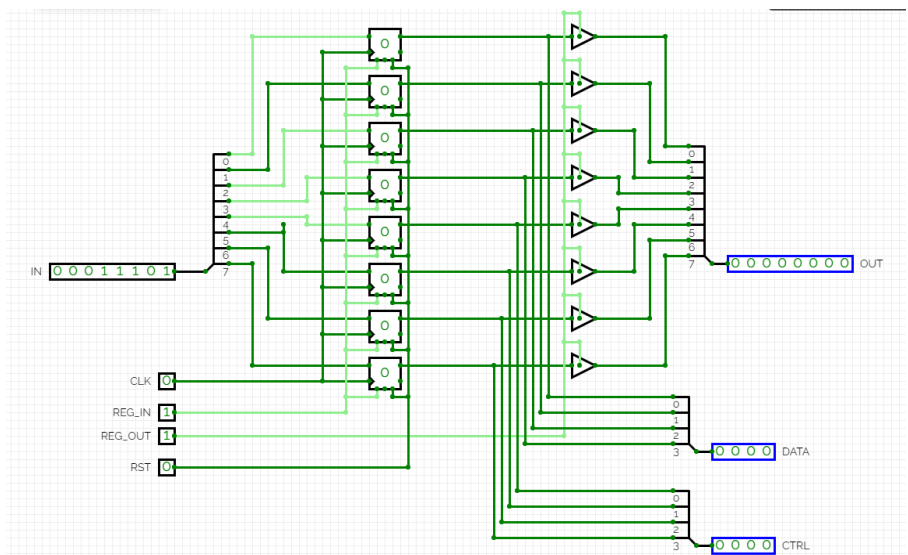2. Instruction Register (reg_IR)

- The instruction register is a part of the control unit.
- To fetch an instruction, the computer does a memory read operation - MEM-OUT
- This places the contents of the addressed memory location on the bus - IR_IN




The design of the instruction register is similar to that of a general CPU register.

However, the input and output lines are different as the output of the instruction register goes to the instruction decoder and not directly to the bus.

 
3. Memory Address Register (reg_MAR)

- As the name suggests, this register stores the 4 - bit address for the corresponding location in the memory.
- The least significant 4 bits correspond to the address.
- The MAR output is directly connected to the address input of the memory.



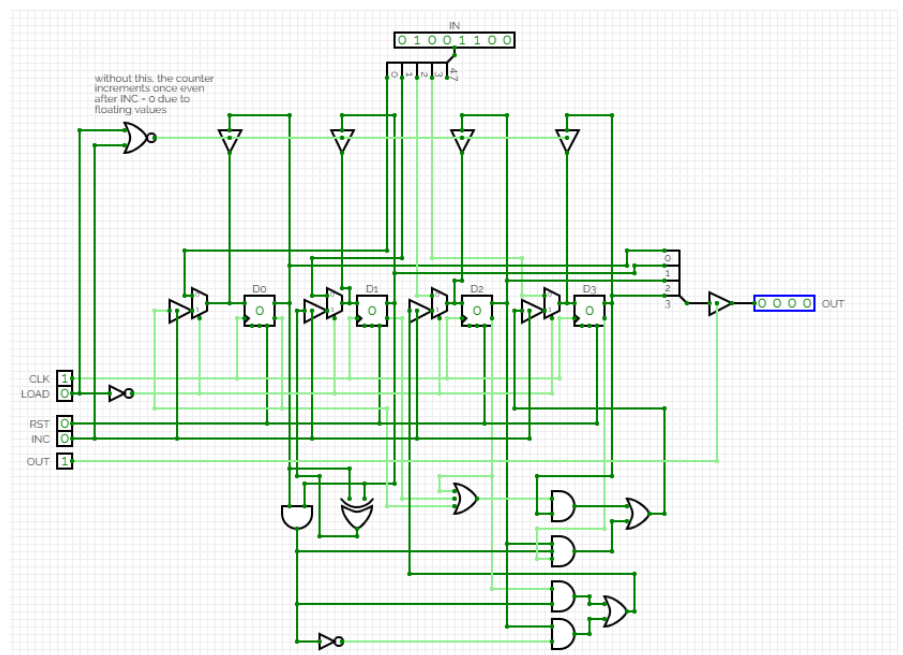4. Program Counter (counter_PC)

- The program is stored at the beginning of memory with the first instruction at 0000, second at 0001 and so on.
- The program counter, which is a part of the control unit, counts from 0000 to 1111.
- It sends the memory address of the next instruction to be fetched and executed.
- It is essentially a pointer which points to the address of the instruction to be executed.



The program counter is reset to 0000 before each computer run (by SYS_RST)

When the computer is run, the program counter sends address 0000 to the memory address register. (PC_OUT and MAR_IN)

The program counter is then incremented to 0001 (PC_INC) simultaneously as the first instruction is read from memory into the instruction register.


This constitutes the fetch cycle.

The first instruction is then executed.

Then address 0001 is sent to the memory address register followed by an increment to 0010 and so on. The second instruction is then executed.

The program counter is thus keeping track of the next instruction to be fetched and executed.

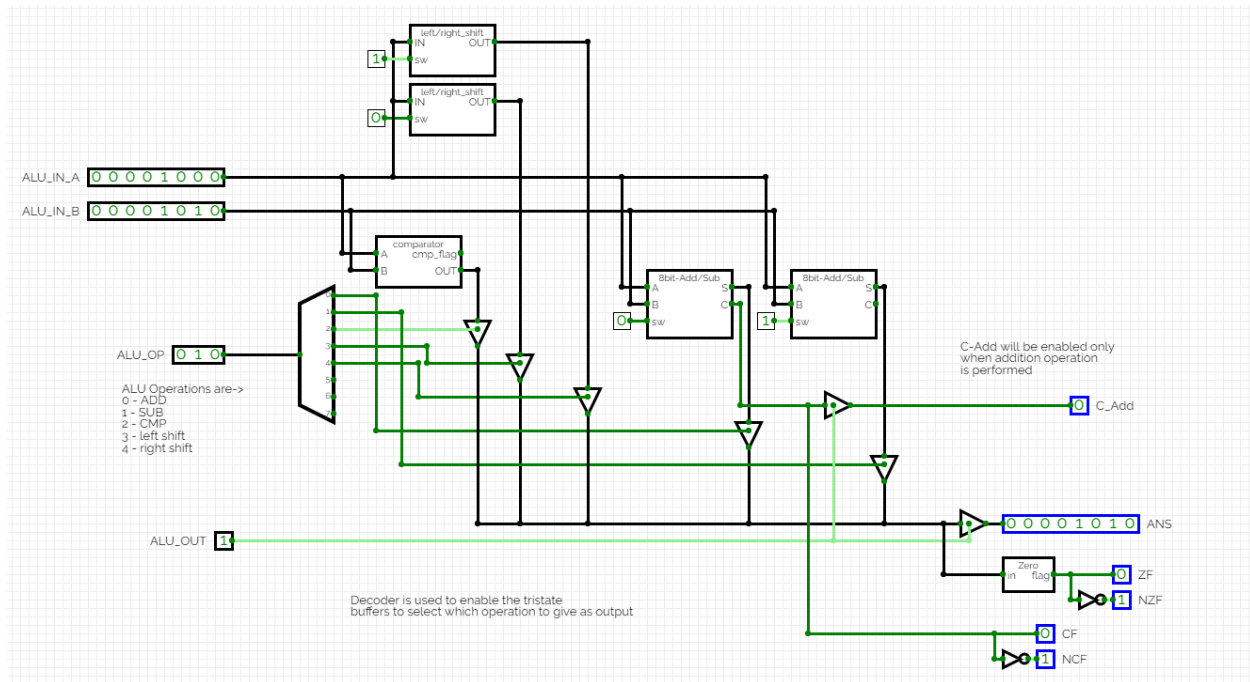5. Arithmetic and Logical Unit (Gajendra_ALU)



ALU is composed of subcircuits for addition, subtraction, left shift, right shift and comparison. It uses a decoder to select one of these 5 operations from the 3 bit ALU_OP.

Zero flag - 1 if answer is 0 by the operation performed in the ALU

Carry flag - 1 if carry is 1 on adding the two inputs A and B


The operations are mapped to the decoder as follows:

- 0 - ADD
- 1 - SUB
- 2 - CMP (Note: outputs A if $A \geq B$, else outputs B)
- 3 - left shift
- 4 - right shift

6. Status Register (reg_status_4)

The status register stores the values of the status flags in the ALU, namely -

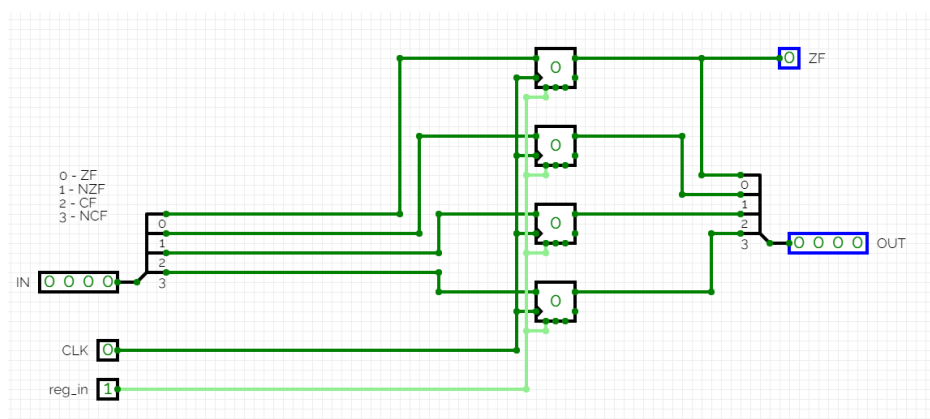- a. Zero Flag
- b. Not Zero Flag
- c. Carry Flag
- d. Not Carry Flag



- The input of the status register are the 4 flag outputs from the ALU
- The status registers takes input only when ALU gives output.
- This is ensured by connecting the reg_in of the status register to the ALU_OUT of the ALU.

INSTRUCTION OP CODES

| NAME | MSBs | LSBs |
|-------|------|------|
| NOP | 0000 | XXXX |
| LDA | 0001 | ADDR |
| STA | 0010 | ADDR |
| ADD | 0011 | ADDR |
| SUB | 0100 | ADDR |
| LDI | 0101 | DATA |
| COUT | 0110 | XXXX |
| JMP | 0111 | ADDR |
| JNZ | 1000 | ADDR |
| SWAP | 1001 | XXXX |
| CMP | 1010 | ADDR |
| LSA | 1011 | XXXX |
| RSA | 1100 | XXXX |
| MOVAB | 1101 | XXXX |
| MOVBC | 1110 | XXXX |
| HALT | 1111 | XXXX |

General execution

<previous instruction>

1010 000 <control word> fetch 1
 1010 001 <control word> fetch 2
 1010 010 <control word> actual stuff 1
 1010 011 <control word> actual stuff 2
 1010 100 <control word> actual stuff 3
 1010 101 <control word> zeros
 1010 110 <control word> zeros
 1010 111 <control word> zeros

<next instruction>

Instruction Set for Gajendra-I

R_A – Register A

R_B – Register B

R_C – Register C

K – Data or address

(K) – Content of memory at address K

1. NOP (No operation)

| | | |
|--|------------------|-------------------------|
| Description: Does not perform any operation. Only fetches the instruction from memory and increments the program counter by 1. | | |
| Operation: No | | |
| Syntax: | Operands: | Program Counter: |
| NOP | None | $PC \leftarrow PC + 1$ |
| 8 bit op code: | | |
| 0000 | 0000 | |

2. LDA

| | | |
|---|--------------------|-------------------------|
| Description: Loads the contents of the addressed memory location into register A. | | |
| Operation: $R_A \leftarrow (K)$ | | |
| Syntax: | Operands: | Program Counter: |
| LDA K | $8 \leq K \leq 15$ | $PC \leftarrow PC + 1$ |
| 8 bit op code: | | |
| 0001 | kkkk | |

3. STA

| | | |
|---|--------------------|-------------------------|
| Description: Loads the contents of register A to the addressed memory location. | | |
| Operation: $(K) \leftarrow R_A$ | | |
| Syntax: | Operands: | Program Counter: |
| STA K | $8 \leq K \leq 15$ | $PC \leftarrow PC + 1$ |
| 8 bit op code: | | |
| 0010 | kkkk | |

(we are using ROM in our implementation, but we have tested STA using a tri-state buffer enabled by mem-in)-(in eeprom we were getting a simulation stack exceeded error)

4. ADD

| | | |
|---|--------------------|-------------------------|
| Description: Adds the contents of the register A with the contents of the addressed memory location and stores the result in register A | | |
| Operation: $R_B \leftarrow (K), R_A \leftarrow R_B + R_A$ | | |
| Syntax: | Operands: | Program Counter: |
| ADD K | $8 \leq K \leq 15$ | $PC \leftarrow PC + 1$ |
| 8 bit op code: | | |
| 0011 | kkkk | |

5. SUB

| | | |
|--|--------------------|-------------------------|
| Description: Subtracts the contents of the register A with the contents of the addressed memory location and stores the result in register A | | |
| Operation: $R_B \leftarrow (K), R_A \leftarrow R_A - R_B$ | | |
| Syntax: | Operands: | Program Counter: |
| SUB K | $8 \leq K \leq 15$ | $PC \leftarrow PC + 1$ |
| 8 bit op code: | | |
| 0100 | kkkk | |

6. LDI

| | | |
|--|--------------------|-------------------------|
| Description: Loads the data given as argument to the instruction to register A | | |
| Operation: $R_A \leftarrow K$ | | |
| Syntax: | Operands: | Program Counter: |
| LDI K | $0 \leq K \leq 15$ | $PC \leftarrow PC + 1$ |
| 8 bit op code: | | |
| 0101 | kkkk | |

7. COUT

| | | |
|--|------------------|-------------------------|
| Description: Outputs the content of register A by first transferring it to register C and displays it on the hex display | | |
| Operation: $R_C \leftarrow R_A$, Display $\leftarrow R_C$ | | |
| Syntax: | Operands: | Program Counter: |
| COUT | None | $PC \leftarrow PC + 1$ |
| 8 bit op code: | | |
| 0110 | xxxx | |

8. JMP

| | | |
|---|---|-------------------------|
| Description: Unconditional jump to the address mentioned in the instruction. Sets program counter to address of instruction | | |
| Operation: None | | |
| Syntax: | Operands: | Program Counter: |
| JMP K | $0 \leq K \leq 7$ (8 memory locations for program and 8 for data but can be varied depending on length of program) | $PC \leftarrow K$ |
| 8 bit op code: | | |
| 0111 | kkkk | |

9. JNZ(Jump Not Zero)

| | | |
|--|---------------------------------|---|
| Description: Conditional jump to the address mentioned in the instruction. Sets program counter to address of instruction if zero flag is not set. | | |
| Operation: None | | |
| Syntax: | Operands: | Program Counter: |
| JNZ K | $0 \leq K \leq 7$ (same as JMP) | $PC \leftarrow K$ (if zero flag not set) $PC \leftarrow PC + 1$ (if zero flag set) |
| 8 bit op code: | | |
| 1000 | kkkk | |

10. SWAP

| | | |
|---|------------------|-------------------------|
| Description: Swaps the contents of register A with register C. | | |
| Operation: $R_B \leftarrow R_A$ $R_A \leftarrow R_C$ $R_C \leftarrow R_B$ | | |
| Syntax: | Operands: | Program Counter: |
| SWAP | None | $PC \leftarrow PC + 1$ |
| 8 bit op code: | | |
| 1001 | xxxx | |

11. CMP

| | | |
|--|--------------------|-------------------------|
| Description: Stores the greater value among the contents of register A and contents of address in register A | | |
| Operation: $R_A \leftarrow K$ (if $R_A < K$) $R_A \leftarrow R_A$ (if $R_A \geq K$) | | |
| Syntax: | Operands: | Program Counter: |
| CMP K | $8 \leq K \leq 15$ | $PC \leftarrow PC + 1$ |
| 8 bit op code: | | |
| 1010 | kkkk | |

12. LSA

| | | |
|--|------------------|-------------------------|
| Description: Left shifts the contents of register A by one bit | | |
| Operation: Logical left shift of 8 bit contents of register A | | |
| Syntax: | Operands: | Program Counter: |
| LSA | None | $PC \leftarrow PC + 1$ |
| 8 bit op code: | | |
| 1011 | xxxx | |

13.RSA

| | | |
|---|------------------|-------------------------|
| Description: Right shifts the contents of register A by one bit | | |
| Operation: Logical right shift of 8 bit contents of register A | | |
| Syntax: | Operands: | Program Counter: |
| RSA | None | $PC \leftarrow PC + 1$ |
| 8 bit op code: | | |
| 1100 | XXXX | |

14.MOVAB

| | | |
|--|------------------|-------------------------|
| Description: Does not perform any operation. Only fetches the instruction from memory and increments the program counter by 1. | | |
| Operation: $R_B \leftarrow R_A$ | | |
| Syntax: | Operands: | Program Counter: |
| MOVAB | None | $PC \leftarrow PC + 1$ |
| 8 bit op code: | | |
| 1101 | XXXX | |

15.MOVBC


| | | |
|--|------------------|-------------------------|
| Description: Does not perform any operation. Only fetches the instruction from memory and increments the program counter by 1. | | |
| Operation: $R_C \leftarrow R_B$ | | |
| Syntax: | Operands: | Program Counter: |
| MOVBC | None | $PC \leftarrow PC + 1$ |
| 8 bit op code: | | |
| 1110 | XXXX | |

16. HALT

| | | |
|--|------------------|-------------------------|
| Description: Stops the program.(stops the clock) | | |
| Operation: No | | |
| Syntax: | Operands: | Program Counter: |
| HALT | None | $PC \leftarrow PC + 1$ |
| 8 bit op code: | | |
| 1111 | XXXX | |

Control Logic and Microinstructions

Software Controller

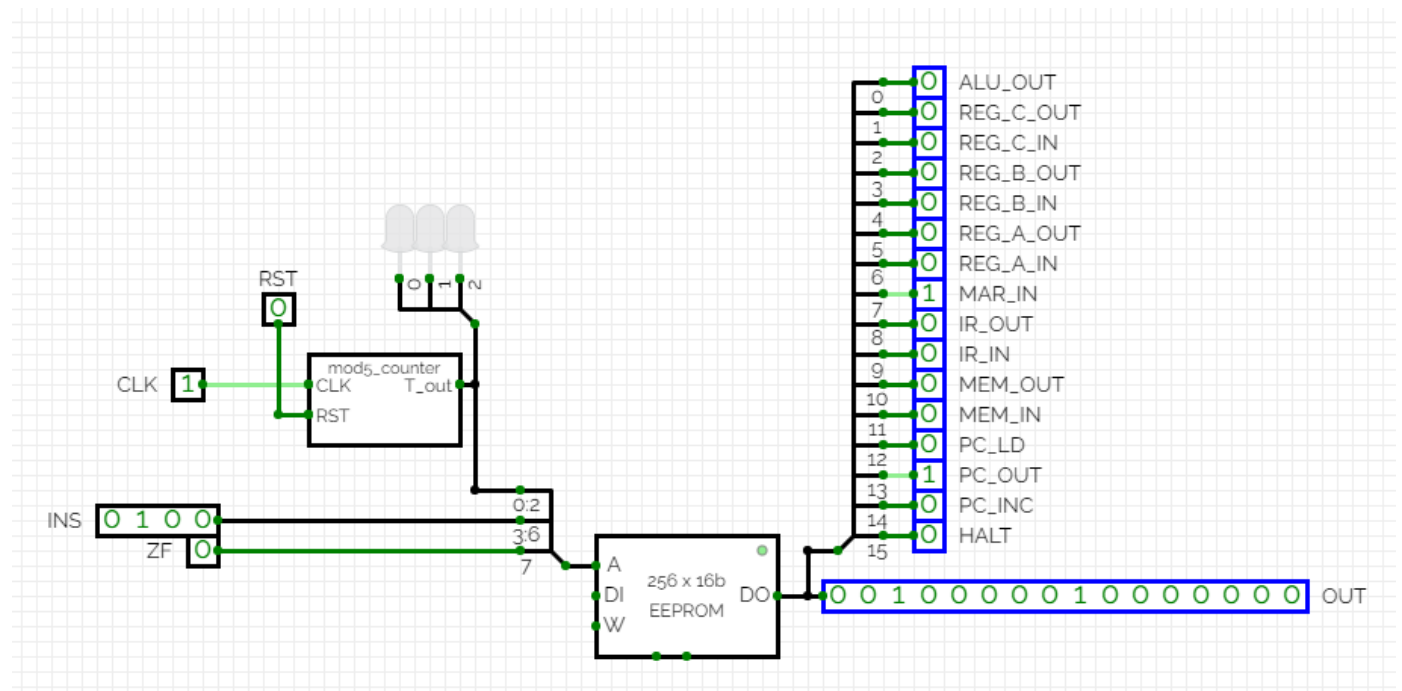

16 bit Control words-
MSB to LSB bit representation.

| | | | | | | | | | | | | | | | |
|------|-----|----|-----|-----|-----|----|-----|--------|-------|-------|-------|-------|-------|-------|-----|
| 15 | 14 | 13 | 12 | 11 | 10 | 9 | 8 | 7 | 6 | 5 | 4 | 3 | 2 | 1 | 0 |
| Halt | PC | PC | PC | MEM | MEM | IR | IR | MAR_IN | REG_A | REG_A | REG_B | REG_B | REG_C | REG_C | ALU |
| | INC | IN | OUT | IN | OUT | IN | OUT | | IN | OUT | IN | OUT | IN | OUT | OUT |

Control words stored in the software controller.

Each instruction has been padded to 8 microinstructions.

Each instruction's T state's control word has to be accessed in memory based on the address given by the instruction along with zero flag and T state.

Each new instruction starts at $8*n$ where n is an integer ≥ 0 .

We have loaded 16 instructions followed by NOPs.

```
0x2080,0x4600,0x0000,0x0000,0x0000,0x0000,0x0000,0x0000,
0x2080,0x4600,0x0180,0x0440,0x0000,0x0000,0x0000,0x0000,
0x2080,0x4600,0x0180,0x0820,0x0000,0x0000,0x0000,0x0000,
0x2080,0x4600,0x0180,0x0410,0x0041,0x0000,0x0000,0x0000,
0x2080,0x4600,0x0180,0x0410,0x0041,0x0000,0x0000,0x0000,
0x2080,0x4600,0x0140,0x0000,0x0000,0x0000,0x0000,0x0000,
0x2080,0x4600,0x0024,0x0002,0x0000,0x0000,0x0000,0x0000,
0x2080,0x4600,0x1100,0x0000,0x0000,0x0000,0x0000,0x0000,
0x2080,0x4600,0x1100,0x0000,0x0000,0x0000,0x0000,0x0000,
0x2080,0x4600,0x0030,0x0042,0x000C,0x0000,0x0000,0x0000,
0x2080,0x4600,0x0180,0x0410,0x0041,0x0000,0x0000,0x0000,
0x2080,0x4600,0x0100,0x0005,0x0042,0x0000,0x0000,0x0000,
0x2080,0x4600,0x0100,0x0005,0x0042,0x0000,0x0000,0x0000,
0x2080,0x4600,0x0030,0x0000,0x0000,0x0000,0x0000,0x0000,
0x2080,0x4600,0x000C,0x0000,0x0000,0x0000,0x0000,0x0000,
0x2080,0x4600,0x8000,0x0000,0x0000,0x0000,0x0000,0x0000,
0x2080,0x4600,0x0000,0x0000,0x0000,0x0000,0x0000,0x0000,
0x2080,0x4600,0x0000,0x0000,0x0000,0x0000,0x0000,0x0000,
0x2080,0x4600,0x0000,0x0000,0x0000,0x0000,0x0000,0x0000,
0x2080,0x4600,0x0000,0x0000,0x0000,0x0000,0x0000,0x0000,
0x2080,0x4600,0x0000,0x0000,0x0000,0x0000,0x0000,0x0000,
0x2080,0x4600,0x0000,0x0000,0x0000,0x0000,0x0000,0x0000,
0x2080,0x4600,0x0000,0x0000,0x0000,0x0000,0x0000,0x0000,
0x2080,0x4600,0x0000,0x0000,0x0000,0x0000,0x0000,0x0000,
0x2080,0x4600,0x0000,0x0000,0x0000,0x0000,0x0000,0x0000,
0x2080,0x4600,0x0000,0x0000,0x0000,0x0000,0x0000,0x0000,
0x2080,0x4600,0x0000,0x0000,0x0000,0x0000,0x0000,0x0000,
0x2080,0x4600,0x0000,0x0000,0x0000,0x0000,0x0000,0x0000,
0x2080,0x4600,0x0000,0x0000,0x0000,0x0000,0x0000,0x0000,
0x2080,0x4600,0x0000,0x0000,0x0000,0x0000,0x0000,0x0000,
```

NOTE:

We have also implemented using FSM, details and pictures of which are at the end of the document.

| Instruction | Control word | T states |
|-------------|-----------------------------------|----------|
| NOP:(0000) | | |
| 2 T states | 1<<PC_OUT 1<<MAR_IN | T1 |
| | 1<<PC_INC 1<<MEM_OUT 1<<IR_IN | T2 |
| | 0 | T3 |
| | 0 | T4 |
| | 0 | T5 |
| LDA:(0001) | | |
| 4 T states | 1<<PC_OUT 1<<MAR_IN | T1 |
| | 1<<PC_INC 1<<MEM_OUT 1<<IR_IN | T2 |
| | 1<<IR_OUT 1<<MAR_IN | T3 |
| | 1<<MEM_OUT 1<<REGA_IN | T4 |
| | 0 | T5 |
| STA:(0010) | | |
| 4 T states | 1<<PC_OUT 1<<MAR_IN | T1 |
| | 1<<PC_INC 1<<MEM_OUT 1<<IR_IN | T2 |
| | 1<<IR_OUT 1<<MAR_IN | T3 |
| | 1<<MEM_IN 1<<REGA_OUT | T4 |
| | 0 | T5 |
| ADD:(0011) | | |
| 5 T states | 1<<PC_OUT 1<<MAR_IN | T1 |
| | 1<<PC_INC 1<<MEM_OUT 1<<IR_IN | T2 |
| | 1<<IR_OUT 1<<MAR_IN | T3 |
| | 1<<MEM_OUT 1<<REGB_IN | T4 |
| | 1<<REGA_IN 1<<ALU_OUT | T5 |

| Instruction | Control word | T states |
|-------------|-----------------------------------|----------|
| SUB:(0100) | | |
| 5 T states | 1<<PC_OUT 1<<MAR_IN | T1 |
| | 1<<PC_INC 1<<MEM_OUT 1<<IR_IN | T2 |
| | 1<<IR_OUT 1<<MAR_IN | T3 |
| | 1<<MEM_OUT 1<<REGB_IN | T4 |
| | 1<<REGA_IN 1<<ALU_OUT | T5 |
| LDI:(0101) | | |
| 3 T states | 1<<PC_OUT 1<<MAR_IN | T1 |
| | 1<<PC_INC 1<<MEM_OUT 1<<IR_IN | T2 |
| | 1<<IR_OUT 1<<REGA_IN | T3 |
| | 0 | T4 |
| | 0 | T5 |
| COUT:(0110) | | |
| 4 T states | 1<<PC_OUT 1<<MAR_IN | T1 |
| | 1<<PC_INC 1<<MEM_OUT 1<<IR_IN | T2 |
| | 1<<REGC_IN 1<<REGA_OUT | T3 |
| | 1<<REGC_OUT | T4 |
| | 0 | T5 |
| JMP:(0111) | | |
| 3 T states | 1<<PC_OUT 1<<MAR_IN | T1 |
| | 1<<PC_INC 1<<MEM_OUT 1<<IR_IN | T2 |
| | 1<<IR_OUT 1<<PC_LOAD | T3 |
| | 0 | T4 |
| | 0 | T5 |

| Instruction | Control word | T states |
|-------------|-----------------------------------|----------|
| JNZ:(1000) | | |
| 3 T states | 1<<PC_OUT 1<<MAR_IN | T1 |
| | 1<<PC_INC 1<<MEM_OUT 1<<IR_IN | T2 |
| | 1<<IR_OUT 1<<PC_LOAD | T3 |
| | 0 | T4 |
| | 0 | T5 |
| SWAP:(1001) | | |
| 5 T states | 1<<PC_OUT 1<<MAR_IN | T1 |
| | 1<<PC_INC 1<<MEM_OUT 1<<IR_IN | T2 |
| | 1<<REGB_IN 1<<REGA_OUT | T3 |
| | 1<<REGA_IN 1<<REGB_OUT | T4 |
| | 1<<REGC_IN 1<<REGB_OUT | T5 |
| CMP:(1010) | | |
| 5 T states | 1<<PC_OUT 1<<MAR_IN | T1 |
| | 1<<PC_INC 1<<MEM_OUT 1<<IR_IN | T2 |
| | 1<<IR_OUT 1<<MAR_IN | T3 |
| | 1<<MEM_OUT 1<<REGB_IN | T4 |
| | 1<<REGA_IN 1<<ALU_OUT | T5 |
| LSA:(1011) | | |
| 5 T states | 1<<PC_OUT 1<<MAR_IN | T1 |
| | 1<<PC_INC 1<<MEM_OUT 1<<IR_IN | T2 |
| | 1<<IR_OUT | T3 |
| | 1<<ALU_OUT 1<<REGC_IN | T4 |
| | 1<<REGA_IN 1<<REGC_OUT | T5 |

| Instruction | Control word | T states |
|-------------|-----------------------------------|----------|
| RSA:(1100) | | |
| 5 T states | 1<<PC_OUT 1<<MAR_IN | T1 |
| | 1<<PC_INC 1<<MEM_OUT 1<<IR_IN | T2 |
| | 1<<IR_OUT | T3 |
| | 1<<ALU_OUT 1<<REGC_IN | T4 |
| | 1<<REGA_IN 1<<REGC_OUT | T5 |
| MOVAB(1101) | | |
| 3 T states | 1<<PC_OUT 1<<MAR_IN | T1 |
| | 1<<PC_INC 1<<MEM_OUT 1<<IR_IN | T2 |
| | 1<<REGA_OUT 1<<REGB_IN | T3 |
| | 0 | T4 |
| | 0 | T5 |
| MOVBC(1110) | | |
| 3 T states | 1<<PC_OUT 1<<MAR_IN | T1 |
| | 1<<PC_INC 1<<MEM_OUT 1<<IR_IN | T2 |
| | 1<<REGC_IN 1<<REGB_OUT | T3 |
| | 0 | T4 |
| | 0 | T5 |
| HALT(1111) | | |
| 3 T states | 1<<PC_OUT 1<<MAR_IN | T1 |
| | 1<<PC_INC 1<<MEM_OUT 1<<IR_IN | T2 |
| | 1<<HALT | T3 |
| | 0 | T4 |
| | 0 | T5 |

Programs

A. Add 2 numbers and display the sum

| | Instruction | Address |
|----|-------------|----------|
| a. | LDA | 0xe → 1e |
| b. | ADD | 0xf → 3f |
| c. | COUT | 0x0 → 60 |

B. Adding and subtracting 4 numbers in some combination

| | | |
|----|------|----------|
| a. | LDA | 0xc → 1c |
| b. | ADD | 0xd → 3d |
| c. | SUB | 0xe → 4e |
| d. | ADD | 0xf → 3f |
| e. | COUT | 0x0 → 60 |

C. Multiplication using repeated addition

| | | | |
|----|-------|----------|---|
| a. | LDA | 0xb → 1b | // store 00 at memory address b(initialising sum) |
| b. | MOVAB | 0x0 → d0 | |
| c. | LDA | 0xd → 1d | // number of times to be added at mem. address d |
| d. | SWAP | 0x0 → 90 | |
| e. | ADD | 0xc → 3c | // number to be added at mem. address c |
| f. | SWAP | 0x0 → 90 | |
| g. | SUB | 0xe → 4e | // store 01 at memory address e |
| h. | SWAP | 0x0 → 90 | |
| i. | JNZ | 0x5 → 85 | |
| j. | COUT | 0x0 → 60 | |

D. Left shift A and display

| | | | |
|----|------|----------|--|
| a. | LDA | 0xb → 1b | // loads register A with contents at b |
| b. | LSA | 0x0 → b0 | //Left shifts contents of register A |
| c. | COUT | 0x0 → 60 | |

E. Compare contents of 2 memory locations and output the larger one

| | | | |
|----|------|----------|---|
| a. | LDA | 0xb → 1b | // loads register A with contents at b |
| b. | CMP | 0xc → ac | //compare register a components and address at c and stores the larger in register a. |
| c. | COUT | 0x0 → 60 | |

FSM controller logic working-

Taken reference from slides and used the states naming convention from the slides.

The controller supports NOP, LDA, STA, ADD, SUB, LDI, JMP, JNZ (will require external logic)

8 inp.

| | | |
|--------|-----|-----|
| 0000 | NOP | 000 |
| 0x7050 | LDA | 001 |
| 0001 | STA | 010 |
| 0x4060 | ADD | 011 |
| 0x0140 | SUB | 100 |
| 0011 | LDI | 101 |
| | JMP | 110 |
| | JMP | 111 |

$D_3 = A$

x
H
2
+
1

| Ins | | | |
|------|-----|------|------|
| 0000 | xxx | 0001 | 0001 |
| 0001 | 000 | 0010 | 0010 |
| 0001 | 001 | 0101 | 0101 |
| 0001 | 010 | 0101 | 0101 |
| 0001 | 011 | 0101 | 0101 |
| 0001 | 100 | 0101 | 0101 |
| 0001 | 101 | 0011 | 0011 |
| 0001 | 110 | 0100 | 0100 |
| 0101 | 001 | 0110 | 0110 |
| 0101 | 010 | 0111 | 0111 |
| 0101 | 011 | 1000 | 1000 |
| 0101 | 100 | 1000 | 1000 |
| 0011 | xxx | 0000 | 0000 |
| 0110 | xxx | 0000 | 0000 |
| 0111 | xxx | 0000 | 0000 |
| 1000 | 011 | 1001 | 1001 |
| 1000 | 100 | 1001 | 1001 |

D_3

$$\begin{aligned} & \overline{P}_3 \overline{P}_2 \overline{P}_1 P_0 \overline{I}_2 I_1 I_0 \\ & + \overline{P}_3 \overline{P}_2 \overline{P}_1 P_0 I_2 \overline{I}_1 \overline{I}_0 \\ & + P_3 \overline{P}_2 \overline{P}_1 \overline{P}_0 I_2 \overline{I}_1 \overline{I}_0 \\ & + P_3 \overline{P}_2 \overline{P}_1 \overline{P}_0 \overline{I}_2 I_1 I_0 \end{aligned}$$

 D_1


$$\begin{aligned} & \overline{P}_3 \overline{P}_2 \overline{P}_1 P_0 \overline{I}_2 \overline{I}_1 \overline{I}_0 \\ & \quad I_2 \overline{I}_1 I_0 \\ & \overline{P}_3 \overline{P}_2 \overline{P}_1 P_0 \overline{I}_2 \overline{I}_1 I_0 \\ & \overline{P}_3 \overline{P}_2 \overline{P}_1 P_0 \overline{I}_2 I_1 \overline{I}_0 \end{aligned}$$


 D_2

$$\begin{aligned} & \overline{P}_3 \overline{P}_2 \overline{P}_1 P_0 \overline{I}_2 \overline{I}_1 I_0 \\ & \overline{P}_3 \overline{P}_2 \overline{P}_1 P_0 \overline{I}_2 I_1 \\ & \overline{P}_3 \overline{P}_2 \overline{P}_1 P_0 I_2 \overline{I}_0 \\ & \overline{P}_3 \overline{P}_2 \overline{P}_1 P_0 \overline{I}_2 I_1 I_0 \\ & P_3 \overline{P}_2 \overline{P}_1 P_0 \overline{I}_2 I_1 \overline{I}_0 \end{aligned}$$

 D_0

$$\begin{aligned} & \overline{P}_3 \overline{P}_2 \overline{P}_1 \overline{P}_0 \\ & + \overline{P}_3 \overline{P}_2 \overline{P}_1 P_0 \overline{I}_2 I_1 \\ & + \overline{P}_3 \overline{P}_2 \overline{P}_1 P_0 \overline{I}_2 \overline{I}_1 \\ & + \overline{P}_3 \overline{P}_2 \overline{P}_1 P_0 \overline{I}_2 I_1 I_0 \\ & + P_3 \overline{P}_2 \overline{P}_1 P_0 \overline{I}_2 I_1 I_0 \\ & + P_3 \overline{P}_2 \overline{P}_1 P_0 I_2 \overline{I}_1 \overline{I}_0 \\ & + \overline{P}_3 \overline{P}_2 \overline{P}_1 P_0 \overline{I}_2 I_1 \overline{I}_0 \end{aligned}$$

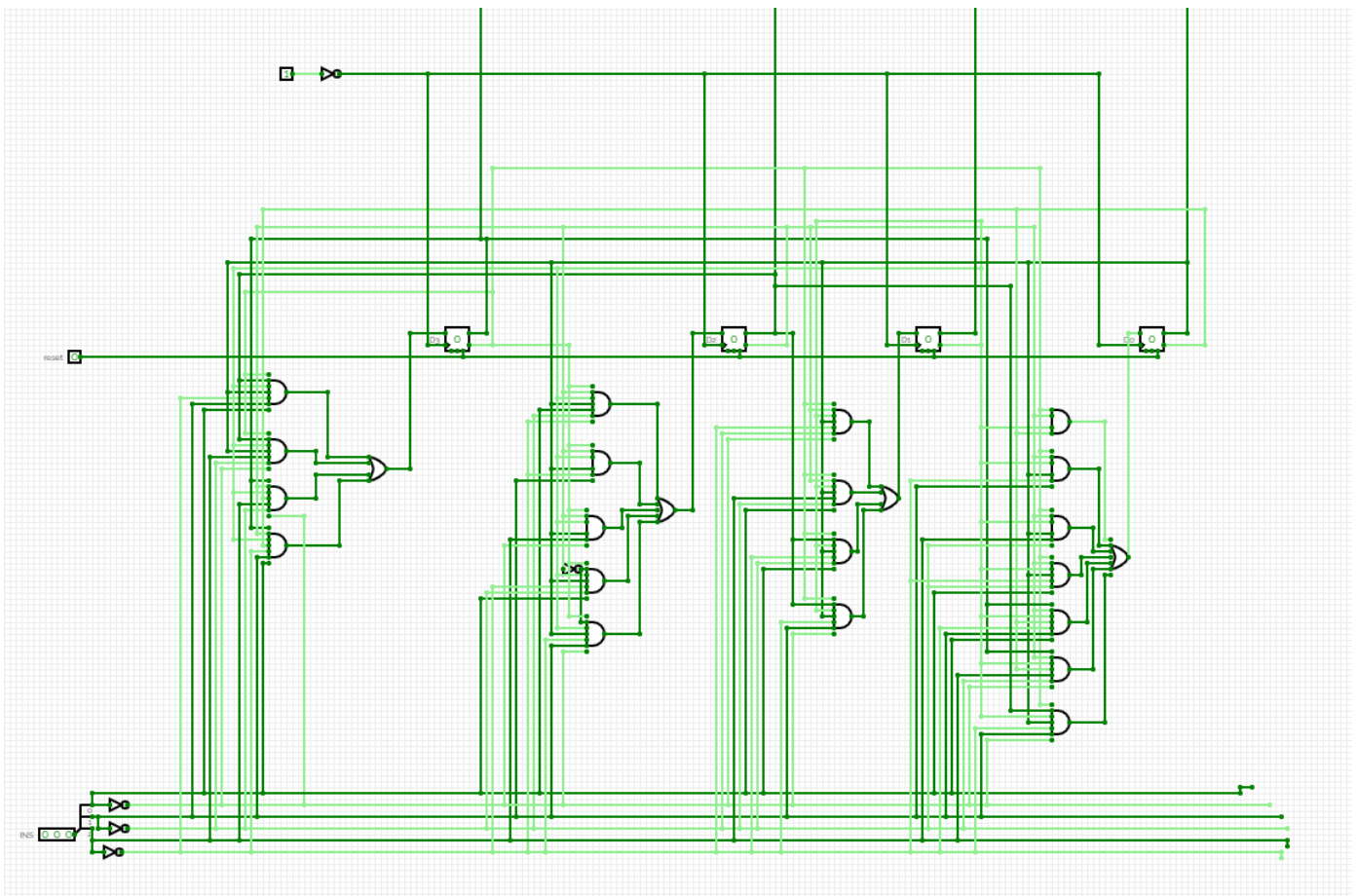

 

FSM is faster because it does not require the additional T-states that were getting wasted in the software controller.

However, it requires more D-flip flops and combinational circuit elements.

We have tested all our components and run different programs to test our circuit.
It was an extremely exciting journey of creating Gajendra-I and we were elated when the programs worked on our homebrew CPU.
Thank you.

END.